

■ CLASS DISCUSSION ITEM 3.7  
**Voltage Limiter**

The diode portion of the following circuit is called a **voltage limiter**. Explain why. Sketch some input and output waveforms that illustrate the circuit's behavior. Note:  $V_H > V_L$ .

