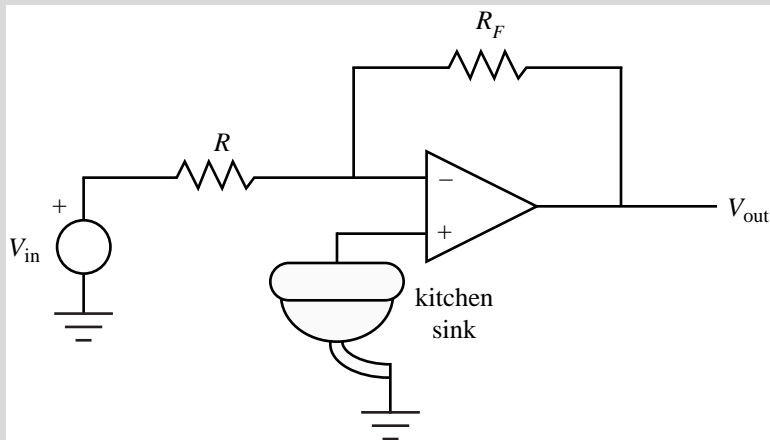


■ CLASS DISCUSSION ITEM 5.1
Kitchen Sink in OP Amp Circuits

Consider the following op amp circuit:



What is the effect of the kitchen sink at the noninverting input of the op amp?