

■ **CLASS DISCUSSION ITEM 5.4**

Integrator Behavior

If a DC voltage is applied as an input to an ideal integrator, how does the output change over time? What is the output given a sinusoidal input? What would the result be if a small DC offset were added to the sinusoidal input?