

■ CLASS DISCUSSION ITEM 6.4

Equivalence of Sum of Products and Product of Sums

Draw the logic circuits for S and C in Example 6.4 using only the product-of-sums results and then do the same for the sum-of-products results. Compare your circuits to the one shown in the example. Also, show that the sum-of-products and product-of-sums results are equivalent.