

■ **CLASS DISCUSSION ITEM 6.7**

Switch Debouncer Function

Track the inputs and outputs of the two NAND gates in Figure 6.17 as the switch moves from contact *B* to contact *A* and create a timing diagram. Also, draw an equivalent circuit for the debouncer using an RS flip-flop.