

Table 6.4 Truth table for the RS flip-flop

Inputs		Outputs	
$S$	$R$	$Q$	$\bar{Q}$
0	0	$Q_0$	$\bar{Q}_0$
1	0	1	0
0	1	0	1
1	1	NA	