

Low-pass Filter

$R := 10000 \cdot \Omega$ resistance

$C := 0.01 \cdot \mu F$ capacitance


$\omega_c := \frac{1}{R \cdot C}$ $\omega_c = (1 \cdot 10^4) \frac{rad}{sec}$ cutoff frequency

$\omega_r = \frac{\omega}{\omega_c}$ frequency ratio

$A(\omega_r) := \frac{1}{\sqrt{1 + \omega_r^2}}$ amplitude ratio as a function of frequency ratio

$A(1) = 0.707$ amplitude ratio at the cutoff frequency

$\omega_r := 0.01, 0.05 \dots 2.5$

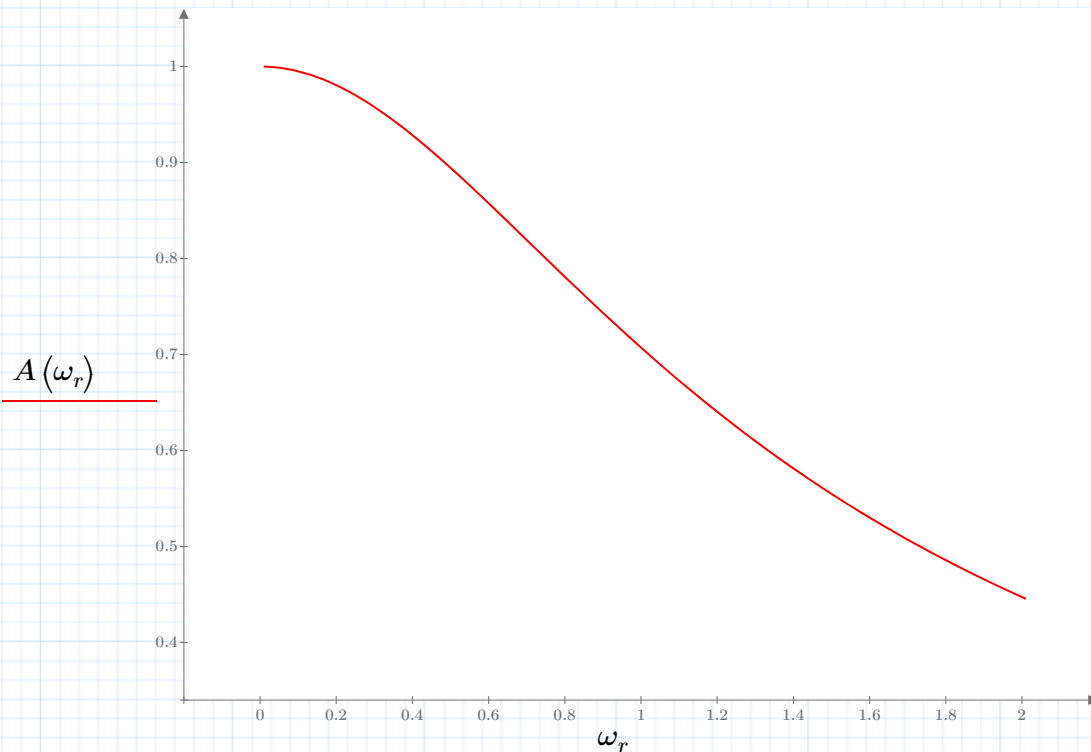

$\phi(\omega_r) := -\text{atan}(\omega_r)$ phase angle as a function of frequency ratio

