LAB 8 QUESTIONS

Group: ____ Names: _____ _____

_____ _____

(1) Which pins of the 7447 should be high to display a "b"?

(2) Draw a schematic of the circuit you used to wire up the normally open (NO) button to reset the counter to 0. Show all required added components and wiring.

(3) When the button is used for the input instead of the 555 circuit, what did you observe with each press and release of the button, and why? Be specific.