

**Lists**

Class Discussion Items	vii
Examples	ix
Design Examples	x
Threaded Design Examples	xi

**Preface**

xiv

Chapter 1**Introduction**

<b>1.1</b>	Mechatronics	1
<b>1.2</b>	Measurement Systems	4
<b>1.3</b>	Threaded Design Examples	5

Chapter 2**Electric Circuits  
and Components**

11

<b>2.1</b>	Introduction	12
<b>2.2</b>	Basic Electrical Elements	14
2.2.1	Resistor	14
2.2.2	Capacitor	20
2.2.3	Inductor	21
<b>2.3</b>	Kirchhoff's Laws	23
2.3.1	Series Resistance Circuit	25
2.3.2	Parallel Resistance Circuit	27
<b>2.4</b>	Voltage and Current Sources and Meters	30
<b>2.5</b>	Thevenin and Norton Equivalent Circuits	35
<b>2.6</b>	Alternating Current Circuit Analysis	37
<b>2.7</b>	Power in Electrical Circuits	44
<b>2.8</b>	Transformer	46
<b>2.9</b>	Impedance Matching	47

**2.10** Practical Considerations

2.10.1	Capacitor Information	50
2.10.2	Breadboard and Prototyping Advice	51
2.10.3	Voltage and Current Measurement	54
2.10.4	Soldering	55
2.10.5	The Oscilloscope	59
2.10.6	Grounding and Electrical Interference	61
2.10.7	Electrical Safety	64

Chapter 3**Semiconductor Electronics**

75

<b>3.1</b>	Introduction	76
<b>3.2</b>	Semiconductor Physics as the Basis for Understanding Electronic Devices	76
<b>3.3</b>	Junction Diode	78
3.3.1	Diode Circuit Applications	82
3.3.2	Optoelectronic Diodes	85
3.3.3	Analysis of Diode Circuits	87
3.3.4	Zener Diode	89
3.3.5	Voltage Regulators	94
<b>3.4</b>	Bipolar Junction Transistor	95
3.4.1	Bipolar Transistor Physics	95
3.4.2	Common Emitter Transistor Circuit	97
3.4.3	Bipolar Transistor Switch	102
3.4.4	Bipolar Transistor Packages	104
3.4.5	Darlington Transistor	105
3.4.6	Phototransistor and Optoisolator	105
<b>3.5</b>	Field-Effect Transistors	107
3.5.1	Behavior of Field-Effect Transistors	108
3.5.2	Symbols Representing Field-Effect Transistors	111
3.5.3	Applications of MOSFETs	112

**Chapter 4****System Response** 123

- 4.1** System Response 124
- 4.2** Amplitude Linearity 124
- 4.3** Fourier Series Representation of Signals 126
- 4.4** Bandwidth and Frequency Response 130
- 4.5** Phase Linearity 135
- 4.6** Distortion of Signals 136
- 4.7** Dynamic Characteristics of Systems 137
- 4.8** Zero-Order System 138
- 4.9** First-Order System 140
  - 4.9.1 Experimental Testing of a First-Order System* 142
- 4.10** Second-Order System 143
  - 4.10.1 Step Response of a Second-Order System* 147
  - 4.10.2 Frequency Response of a System* 149

**4.11 System Modeling and Analogies** 156**Chapter 5****Analog Signal Processing Using Operational Amplifiers** 168

- 5.1** Introduction 169
- 5.2** Amplifiers 169
- 5.3** Operational Amplifiers 171
- 5.4** Ideal Model for the Operational Amplifier 171
- 5.5** Inverting Amplifier 174
- 5.6** Noninverting Amplifier 176
- 5.7** Summer 180
- 5.8** Difference Amplifier 180
- 5.9** Instrumentation Amplifier 183
- 5.10** Integrator 185
- 5.11** Differentiator 186
- 5.12** Sample and Hold Circuit 187
- 5.13** Comparator 188
- 5.14** The Real Op Amp 189
  - 5.14.1 Important Parameters from Op Amp Data Sheets* 191

**Chapter 6****Digital Circuits** 205

- 6.1** Introduction 206
- 6.2** Digital Representations 207
- 6.3** Combinational Logic and Logic Classes 210
- 6.4** Timing Diagrams 213
- 6.5** Boolean Algebra 214
- 6.6** Design Of Logic Networks 216
  - 6.6.1 Define the Problem in Words* 216
  - 6.6.2 Write Quasi-Logic Statements* 217
  - 6.6.3 Write the Boolean Expression* 217
  - 6.6.4 AND Realization* 218
  - 6.6.5 Draw the Circuit Diagram* 218
- 6.7** Finding a Boolean Expression Given a Truth Table 219
- 6.8** Sequential Logic 222
- 6.9** Flip-Flops 222
  - 6.9.1 Triggering of Flip-Flops* 224
  - 6.9.2 Asynchronous Inputs* 226
  - 6.9.3 D Flip-Flop* 227
  - 6.9.4 JK Flip-Flop* 227
- 6.10** Applications of Flip-Flops 230
  - 6.10.1 Switch Debouncing* 230
  - 6.10.2 Data Register* 231
  - 6.10.3 Binary Counter and Frequency Divider* 232
  - 6.10.4 Serial and Parallel Interfaces* 232
- 6.11** TTL and CMOS Integrated Circuits 234
  - 6.11.1 Using Manufacturer IC Data Sheets* 236
  - 6.11.2 Digital IC Output Configurations* 238
  - 6.11.3 Interfacing TTL and CMOS Devices* 240
- 6.12** Special Purpose Digital Integrated Circuits 243
  - 6.12.1 Decade Counter* 243
  - 6.12.2 Schmitt Trigger* 247
  - 6.12.3 555 Timer* 248
- 6.13** Integrated Circuit System Design 253
  - 6.13.1 IEEE Standard Digital Symbols* 257

**Chapter 7****Microcontroller Programming  
and Interfacing** 266

- 7.1** Microprocessors and Microcomputers 267
- 7.2** Microcontrollers 269
- 7.3** The PIC16F84 Microcontroller 273
- 7.4** Programming a PIC 276
- 7.5** Picbasic Pro 282
  - 7.5.1 PicBasic Pro Programming Fundamentals* 282
  - 7.5.2 PicBasic Pro Programming Examples* 291
- 7.6** Using Interrupts 304
- 7.7** The Arduino Prototyping Platform 308
- 7.8** Interfacing Common PIC Peripherals 318
  - 7.8.1 Numeric Keypad* 319
  - 7.8.2 LCD Display* 321
- 7.9** Interfacing to the PIC 326
  - 7.9.1 Digital Input to the PIC* 328
  - 7.9.2 Digital Output from the PIC* 329
- 7.10** Serial Communication 330
- 7.11** Method to Design a Microcontroller-Based System 337
- 7.12** Practical Considerations 363
  - 7.12.1 PIC Project Debugging Procedure* 364
  - 7.12.2 Power Supply Options for PIC Projects* 365
  - 7.12.3 Battery Characteristics* 368
  - 7.12.4 Other Considerations for Project Prototyping and Design* 371

**Chapter 8****Data Acquisition** 376

- 8.1** Introduction 377
- 8.2** Reconstruction of Sampled Signals 381
- 8.3** Quantizing Theory 384
- 8.4** Analog-to-Digital Conversion 385
  - 8.4.1 Introduction* 385
  - 8.4.2 Analog-to-Digital Converters* 388
- 8.5** Digital-to-Analog Conversion 391

- 8.6** Virtual Instrumentation, Data Acquisition, and Control 395
- 8.7** Practical Considerations 399

- 8.7.1 Introduction to LabVIEW Programming* 399
- 8.7.2 The USB 6009 Data Acquisition Module* 401
- 8.7.3 Creating a VI and Sampling Music* 403

**Chapter 9****Sensors** 409

- 9.1** Introduction 410
- 9.2** Position and Speed Measurement 410
  - 9.2.1 Proximity Sensors and Switches* 411
  - 9.2.2 Potentiometer* 413
  - 9.2.3 Linear Variable Differential Transformer* 414
  - 9.2.4 Digital Optical Encoder* 417
- 9.3** Stress and Strain Measurement 425
  - 9.3.1 Electrical Resistance Strain Gage* 426
  - 9.3.2 Measuring Resistance Changes with a Wheatstone Bridge* 430
  - 9.3.3 Measuring Different States of Stress with Strain Gages* 434
  - 9.3.4 Force Measurement with Load Cells* 439
- 9.4** Temperature Measurement 441
  - 9.4.1 Liquid-in-Glass Thermometer* 442
  - 9.4.2 Bimetallic Strip* 442
  - 9.4.3 Electrical Resistance Thermometer* 442
  - 9.4.4 Thermocouple* 443
- 9.5** Vibration and Acceleration Measurement 448
  - 9.5.1 Piezoelectric Accelerometer* 455
- 9.6** Pressure and Flow Measurement 459
- 9.7** Semiconductor Sensors and Microelectromechanical Devices 459

**Chapter 10****Actuators** 465

- 10.1** Introduction 466
- 10.2** Electromagnetic Principles 466

<b>10.3</b>	Solenoids and Relays	467
<b>10.4</b>	Electric Motors	469
<b>10.5</b>	DC Motors	475
	<i>10.5.1 DC Motor Electrical Equations</i>	478
	<i>10.5.2 Permanent Magnet DC Motor Dynamic Equations</i>	479
	<i>10.5.3 Electronic Control of a Permanent Magnet DC Motor</i>	481
	<i>10.5.4 Bidirectional DC Motor Control</i>	483
<b>10.6</b>	Stepper Motors	489
	<i>10.6.1 Stepper Motor Drive Circuits</i>	496
<b>10.7</b>	RC Servo Motors	499
<b>10.8</b>	Selecting a Motor	501
<b>10.9</b>	Hydraulics	506
	<i>10.9.1 Hydraulic Valves</i>	508
	<i>10.9.2 Hydraulic Actuators</i>	510
<b>10.10</b>	Pneumatics	512

**Chapter 11****Mechatronic Systems—Control Architectures and Case Studies** 516

<b>11.1</b>	Introduction	517
<b>11.2</b>	Control Architectures	517
	<i>11.2.1 Analog Circuits</i>	517
	<i>11.2.2 Digital Circuits</i>	518
	<i>11.2.3 Programmable Logic Controller</i>	518
	<i>11.2.4 Microcontrollers and DSPs</i>	520
	<i>11.2.5 Single-Board Computer</i>	521
	<i>11.2.6 Personal Computer</i>	521
<b>11.3</b>	Introduction to Control Theory	521
	<i>11.3.1 Armature-Controlled DC Motor</i>	522
	<i>11.3.2 Open-Loop Response</i>	524

	<i>11.3.3 Feedback Control of a DC Motor</i>	525
	<i>11.3.4 Controller Empirical Design</i>	528
	<i>11.3.5 Controller Implementation</i>	529
	<i>11.3.6 Conclusion</i>	531
<b>11.4</b>	Case Studies	532
	<i>11.4.1 Myoelectrically Controlled Robotic Arm</i>	532
	<i>11.4.2 Mechatronic Design of a Coin Counter</i>	545
	<i>11.4.3 Mechatronic Design of a Robotic Walking Machine</i>	554
<b>11.5</b>	List of Various Mechatronic Systems	559

**Appendix A****Measurement Fundamentals** 561

<b>A.1</b>	Systems of Units	561
	<i>A.1.1 Three Classes of SI Units</i>	563
	<i>A.1.2 Conversion Factors</i>	565
<b>A.2</b>	Significant Figures	566
<b>A.3</b>	Statistics	568
<b>A.4</b>	Error Analysis	571
	<i>A.4.1 Rules for Estimating Errors</i>	572

**Appendix B****Physical Principles** 574

<b>Appendix C</b>		
<b>Mechanics of Materials</b>		579

<b>C.1</b>	Stress and Strain Relations	579
------------	-----------------------------	-----

**Index** 583